
Kit No     Date:	TXIL INO.	Date:	1		U1244 56789 msfill-1pt 301M	
------------------	-----------	-------	---	--	-----------------------------------	--

## LABORATORY 1

Please print this sheet prior to coming to laboratory. Complete the pre-laboratory tasks in your lab notebook. Complete the lab tasks in **both** your lab notebook and this submission sheet.

## 1 Pre-laboratory Verification

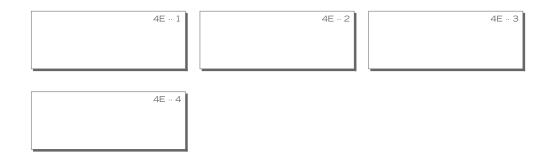

## 2 Laboratory Verification



## 3 Deliverables

1. Copy the results table below (you may omit **0** values):

Base-2	Base-10	Calculated V <sub>out</sub> (V)	<b>Measured</b> Vout (V)	$  (\mathbf{M} - \mathbf{C})/\mathbf{C} * 100\%  $
0000	0	0		_
0001	1	0.333		
0010	2			
0011	3			
0100				
0101				
0110				
0111				
1000				
1001				
1010				
1011				
1100				
1101				
1110				
1111				

_				1																									_	
2.	E	xpl	lain	ı w	hat	the	e re	sul	ts t	able	e re	epre	ese	nts:																
												•																		
				٠										٠		٠			٠											
		٠				٠	٠		٠		٠	٠	٠	٠	٠	٠	٠	٠	٠			٠	٠	٠						
	•	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠			
	•	•	٠	•	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	•	٠	٠	٠			
	•	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠	٠			
				٠	٠					٠		٠	٠	٠	٠	٠	٠	٠	٠	٠	٠				٠					
		-		-	rint fre							-		apt	ure	to	the	su	bm	iss	ion	. Ir	ndio	cate	e th	e c	alcu	late	d m	ag
	M	ag	nit	ude	e:																				-					_ \
	Fı	eq	uer	псу	·:																				_					H