


| | |
|--|--|
| | |
|--|--|

| | | | | | | | |
|--|--|---|--|--|---|--|--|
| | | / | | | / | | |
|--|--|---|--|--|---|--|--|

USE TEMPLATE

| | | | | |
|---|---|---|---|---|
| 0 | 1 | 2 | 3 | 4 |
| 5 | 6 | 7 | 8 | 9 |

MISFILL -1 PT

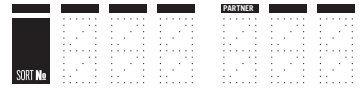

Please print this sheet prior to coming to laboratory. Complete the pre-laboratory tasks in your lab notebook. Complete the lab tasks in **both** your lab notebook and this submission sheet.

1 Pre-laboratory Verification


[illegible]

2 Laboratory Verification

Two empty rectangular boxes are provided for drawing. The left box is labeled "4E .. 24" at the top right corner. The right box is labeled "4E .. 25" at the top right corner.

3 Deliverables

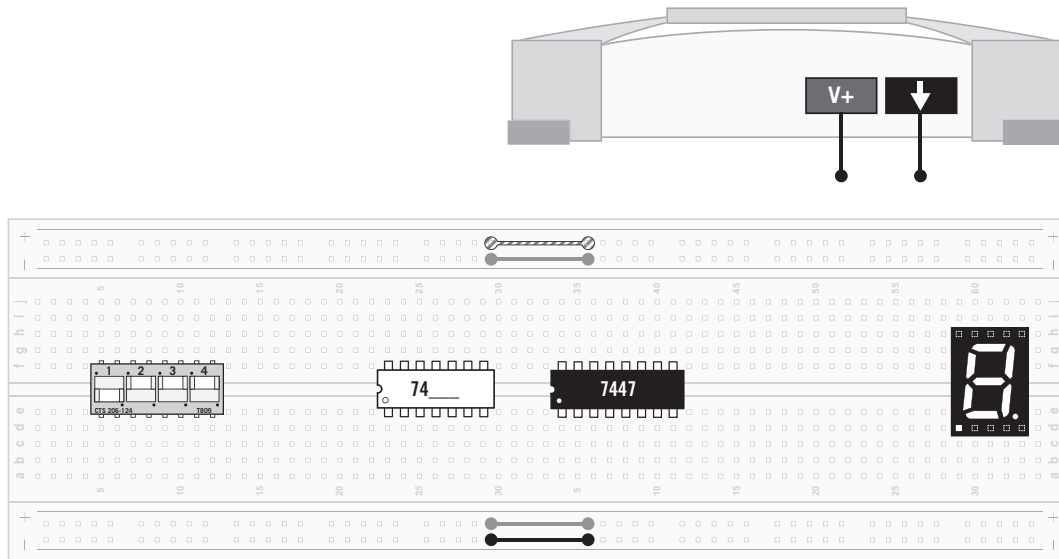1. Draw the circuit that you used to implement the blanking circuitry:



2. What is the purpose of creating a blanking circuit for the seven-segment display?

3. How would one create a combinational circuit to light the center bar (G) of the seven-segment display (resulting in a dash) instead of only blanking it? **Explain the process.**