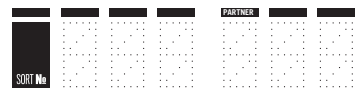


Kit No. Date: / /

USE TEMPLATE
01234
56789
MISFILL -1 PT



LABORATORY 2

Please print this sheet prior to coming to laboratory. Complete the pre-laboratory tasks in your lab notebook. Complete the lab tasks in **both** your lab notebook and this submission sheet.

1 Pre-laboratory Verification

<div>4E .. 8</div>	<div>4E .. 9</div>	<div>4E .. 10</div>
<div>4E .. 11</div>	<div>4E .. 12</div>	

2 Laboratory Verification

<div>4E .. 13</div>

3 Deliverables

1. Copy the results table below (you may omit **0** values):

Base 2	Base 10	Calculated V_{in} (V)	INPUT		OUTPUT	
			Measured V_{in} (V)	Level (low/high)*	Measured V_{out} (V)	Level (low/high)*
0000	0	0.000				
0001	1	0.220				
0010	2	0.440				
0011	3	0.660				
0100	4	0.880				
0101	5	1.100				
0110	6	1.320				
0111	7	1.540				
1000	8	1.760				
1001	9	1.980				
1010	10	2.200				
1011	11	2.420				
1100	12	2.640				
1101	13	2.860				
1110	14	3.080				
1111	15	3.300				

* Based on IC datasheet values of V_{IH} , V_{IL} , V_{OH} , and V_{OL} .

2. Explain what the results table represents. Focus especially on the logic levels and why the readings make sense (or don't).

.....

.....

.....

.....

.....

.....

3. What can you observe from the plot of the results?

.....

.....

.....

.....

.....

.....

4. Staple a printout of the plot to this submission sheet.