

Kit No. Date: / /

USE TEMPLATE
01234
56789
MISFILL -1 PT



LABORATORY 3

Please print this sheet prior to coming to laboratory. Complete the pre-laboratory tasks in your lab notebook. Complete the lab tasks in **both** your lab notebook and this submission sheet.

1 Pre-laboratory Verification

<div>4E .. 14</div> <div></div>	<div>4E .. 15</div> <div></div>	<div>4E .. 16</div> <div></div>
<div>4E .. 17</div> <div></div>	<div>4E .. 18</div> <div></div>	

2 Laboratory Verification

<div>4E .. 19</div> <div></div>	<div>4E .. 20</div> <div></div>
---------------------------------	---------------------------------

3 Deliverables

1. Copy the results table below (you may omit **0** values):

Inputs			Predicted					74XX					Simulated					FPGA				
			Intermediate				F	Intermediate				F	Intermediate				F	Intermediate				F
A	B	C	net3	net2	net1	net0		net3	net2	net1	net0		net3	net2	net1	net0		net3	net2	net1	net0	
0	0	0																				
0	0	1																				
0	1	0																				
0	1	1																				
1	0	0																				
1	0	1																				
1	1	0																				
1	1	1																				

2. Compare circuit output results between predictions, 74XX (IC) implementation, Quartus simulation, and FPGA hardware. Are the results identical? **Explain why or why not.**

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....

3. Interpret the laboratory data in the context of the circuit. Does the behavior of the output make sense, given the components used? **Explain.**

.....

.....

.....

.....

.....

.....

.....

.....

.....

.....